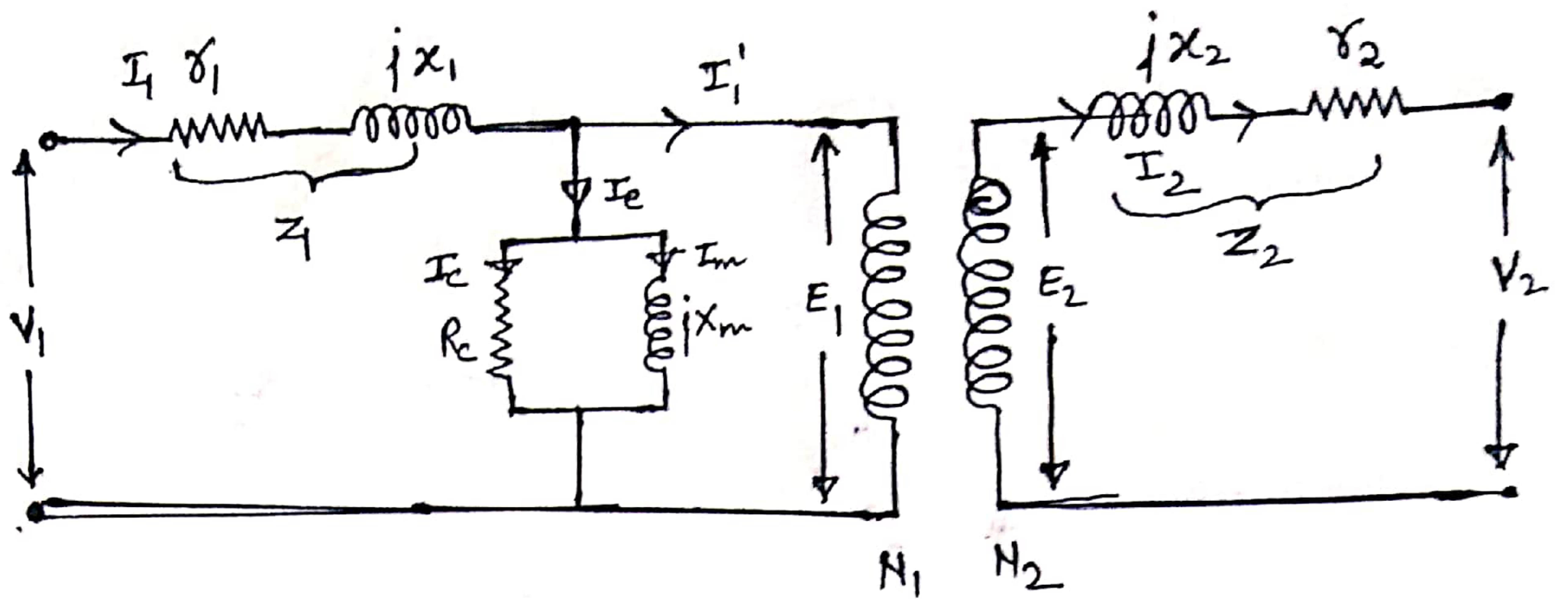


4.11 Equivalent Circuit of a transformer.



$r_1 \rightarrow$ Resistance of Primary winding

$x_1 \rightarrow$ ^{leakage} Reactance of Primary winding

$I_e \rightarrow$ No load current or exciting current

$I_c \rightarrow$ Core loss current

$I_m \rightarrow$ magnetizing current

$R_c \rightarrow$ core loss resistance

$X_m \rightarrow$ magnetizing reactance

$r_2 \rightarrow$ Resistance of Secondary winding


$x_2 \rightarrow$ Leakage reactance of secondary winding

$Z_1 = (r_1 + jx_1) \rightarrow$ impedance of primary winding

$Z_2 = (r_2 + jx_2) \rightarrow$ impedance of secondary winding

4.11 Equivalent Circuit of a Transformer, Continued -


(a) Concept of leakage reactance

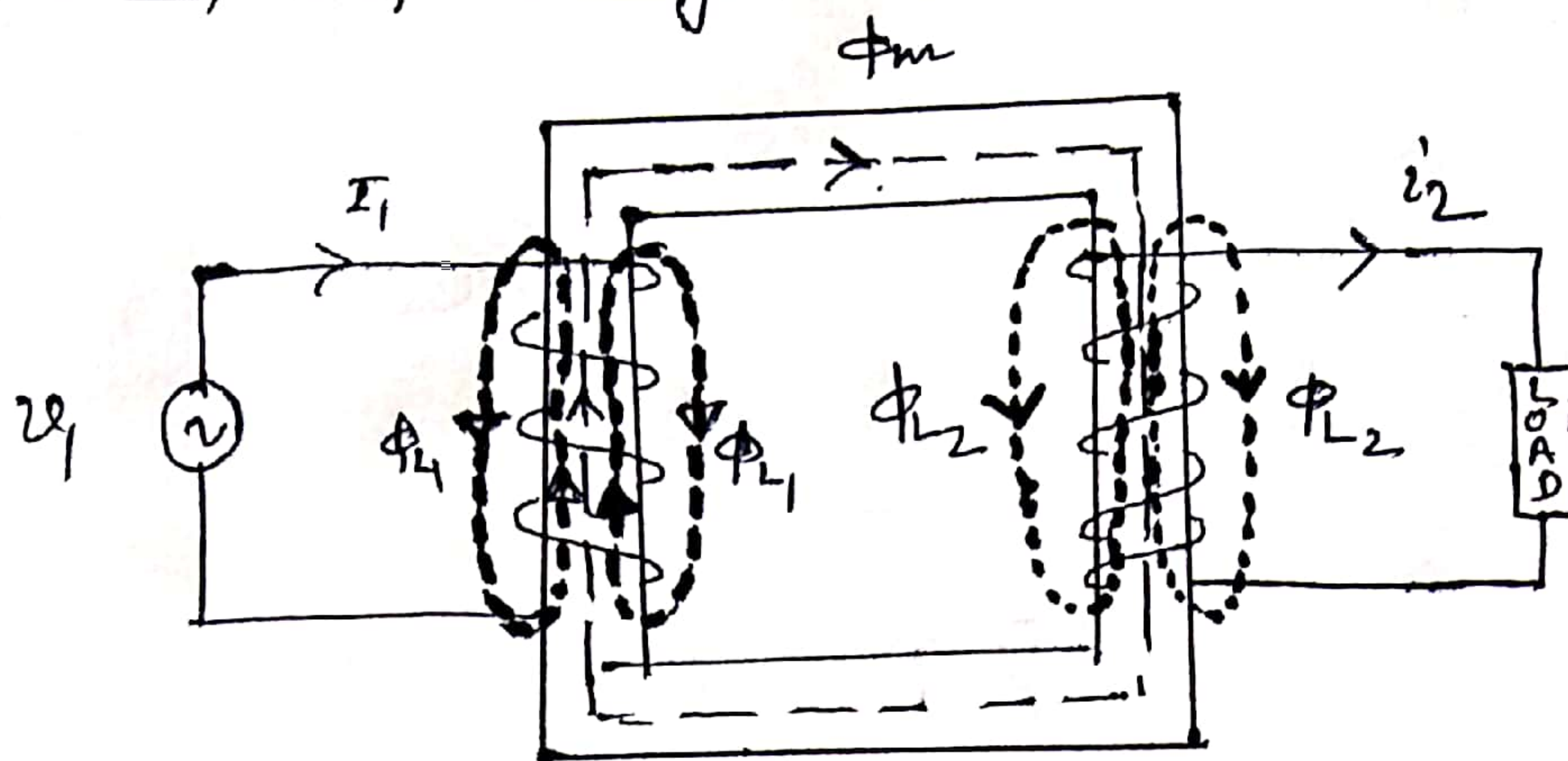

- (i) Part of the total flux of a winding that links only with the winding itself and/or metallic body parts of transformer such as tank wall, core clamps etc. is called leakage flux.

Φ_{L1} & Φ_{L2} are leakage flux associated with primary and secondary winding respectively

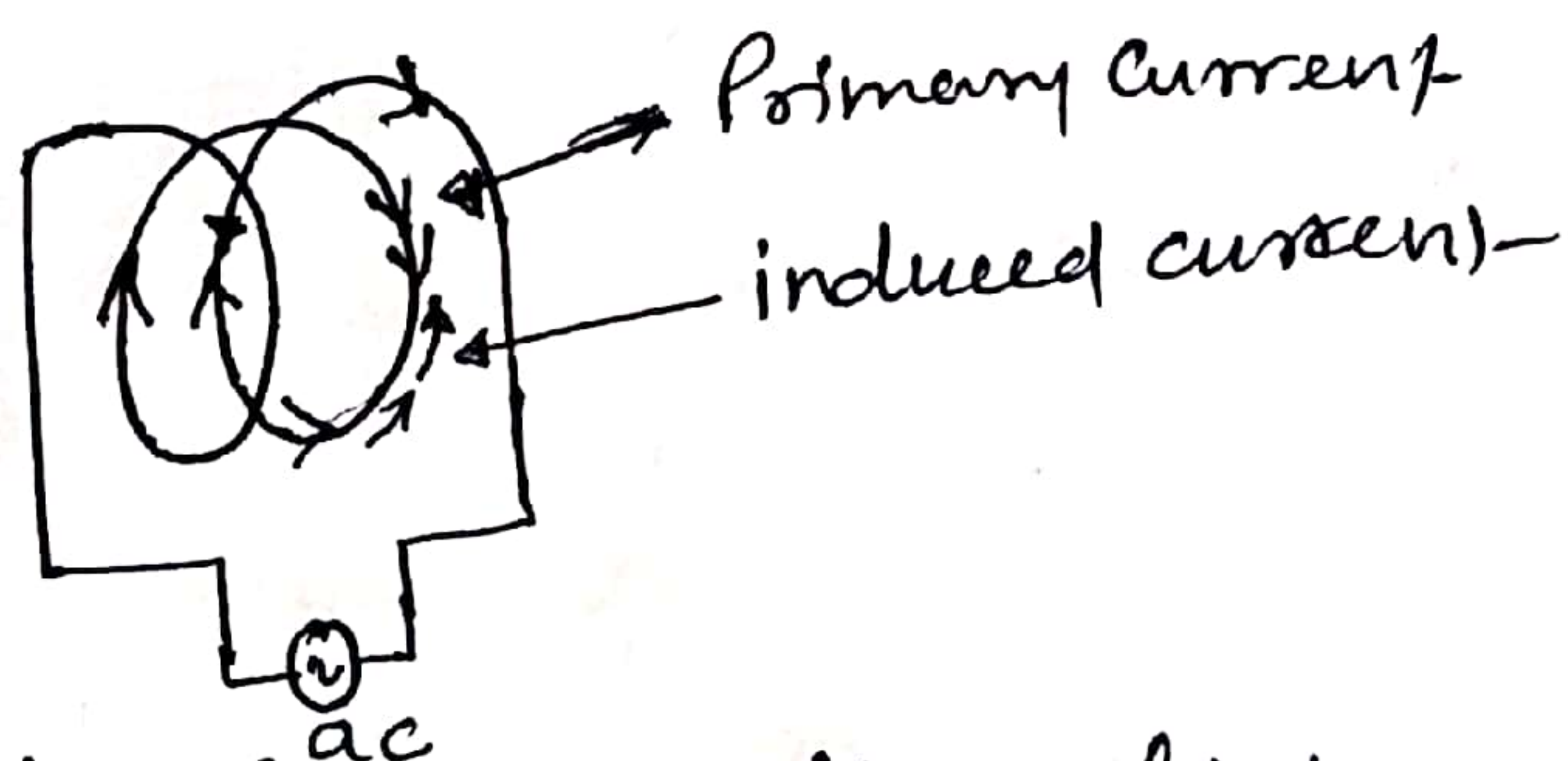- (ii) Part of total flux linking both winding on HV and LV side is called mutual flux Φ_m .




- (iii) Since time varying leakage flux links with the concerned winding itself, by electromagnetic induction it induces an emf (effect) through self induction in order to oppose the cause i.e. time varying current that created leakage flux.

An electrical element that exhibits this property of self-inductance is an inductor. That's why inductor is used to account for effect of leakage flux in the form of inductive reactance in the model circuit.

⑥ Concept of shunt branch :

- The shunt resistance in the transformer equivalent circuit represents the loss taking place in the core.
- The shunt inductance represents the magnetising component.
- Actually when current is passed through primary winding some of the total current is used up to produce the working magnetic field and some current is used up as heat dissipation in the core of the transformer. The magnetic field production is represented as some current flowing through a pure inductor (shunt) producing the working magnetic field. The core loss is represented through some heat dissipation due to current flowing through a fictitious resistance (shunt core resistance).
- Now as out of the total current flowing into the transformer primary, only a part is consumed as core loss component and magnetising component, thus these components are required to be represented separately from the remaining current which flows in series and is used to transfer electric power from primary to secondary. And we know that current gets divided into two components in a network having two shunt branches. Thus shunt (parallel) representation allows to separate the core loss and magnetising component of current from remaining total current in the Primary.

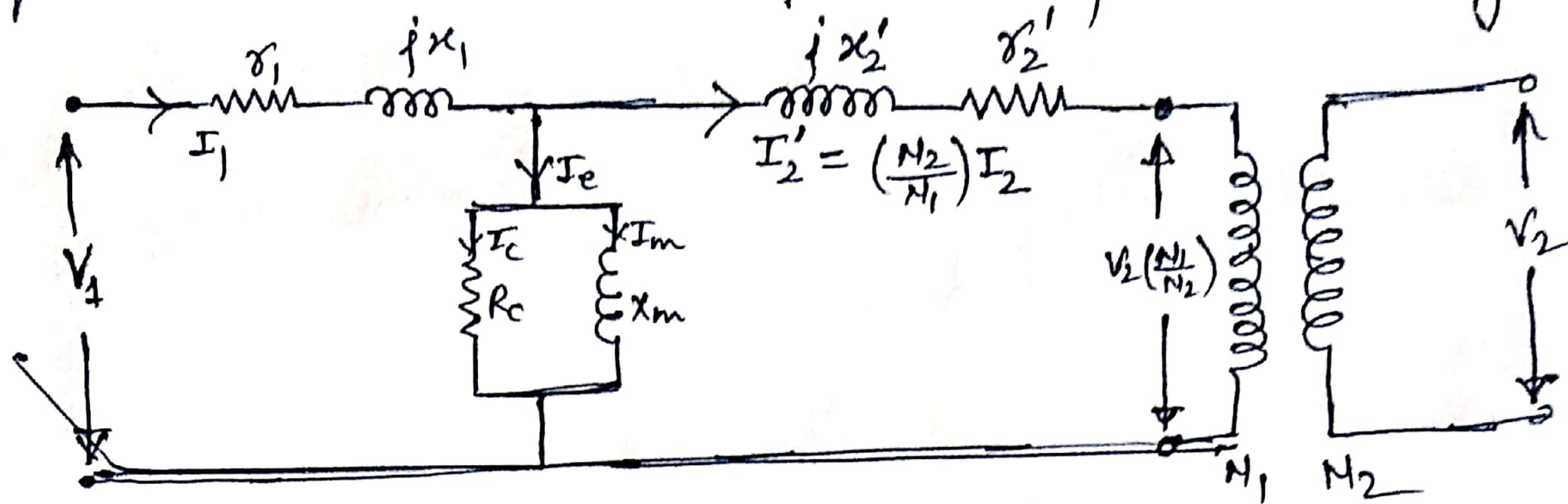(c) Equivalent circuit when secondary circuit referred to Primary



Total equivalent resistance referred to Primary -

$$r_{e1} = r_1 + r_2' = r_1 + \left(\frac{N_1}{N_2}\right)^2 r_2$$


Total equivalent leakage reactance referred to Primary

$$x_{e1} = x_1 + x_2' = x_1 + \left(\frac{N_1}{N_2}\right)^2 x_2$$

Total equivalent impedance referred to Primary

$$Z_{e1} = r_{e1} + jx_{e1}$$

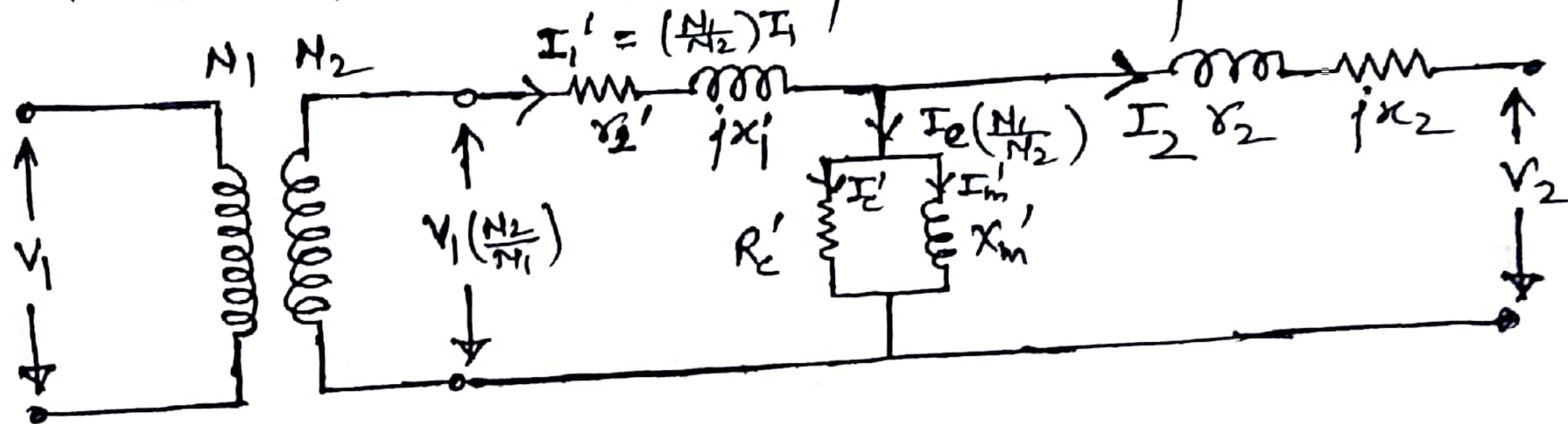(d) Equivalent circuit when Primary circuit referred to ~~Primary~~ ^{Secondary}



Total equivalent resistance referred to Secondary

$$r_{e2} = r_2 + r_1' = r_2 + \left(\frac{N_2}{N_1}\right)^2 r_1$$

Total equivalent leakage reactance -

$$x_{e2} = x_2 + x_1' = x_2 + \left(\frac{N_2}{N_1}\right)^2 x_1$$

Total impedance -

$$Z_{e2} = r_{e2} + jx_{e2}$$

4.12 Phasor diagram of an ideal transformer at No load

* $\phi = \phi_m \sin \omega t \rightarrow$ Common to both Primary and secondary — (1)

$$E_1 = E_{1\max} \sin(\omega t - \frac{\pi}{2}) \text{ — (2)}$$

$$E_2 = E_{2\max} \sin(\omega t - \frac{\pi}{2}) \text{ — (3)}$$


$$V_1 = -E_1 \text{ — (4)}$$

exciting / No load Current $I_0 = I_c + I_m$ — (5)

For No load $I_2 = 0$

$$I_1 = I_0$$


$$V_2 = E_2 \text{ — (6)}$$

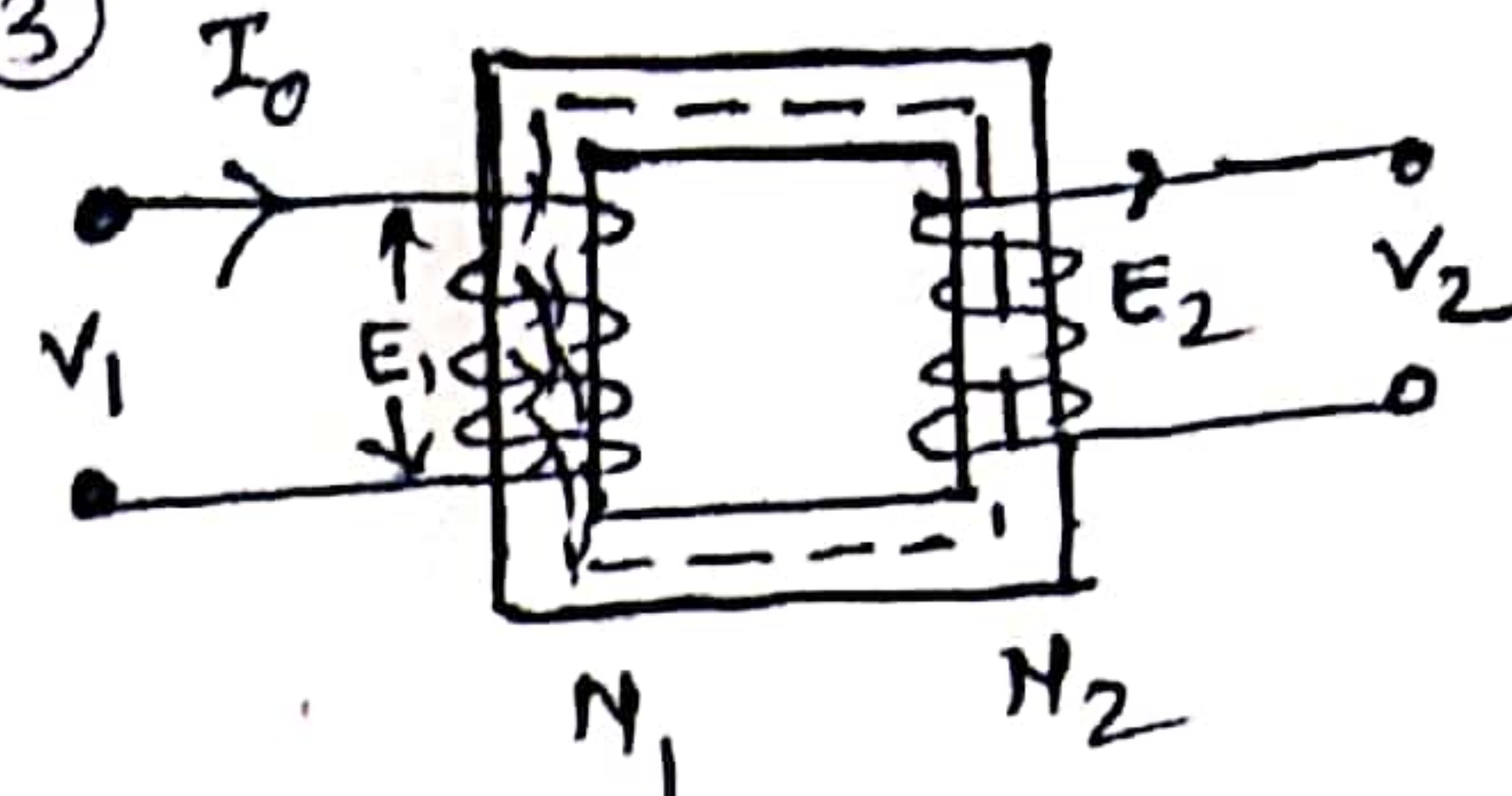

Here $N_1 = N_2$

$I_m \rightarrow$ is the reactive or magnetizing current - since its function is to provide the required magnetic flux ϕ

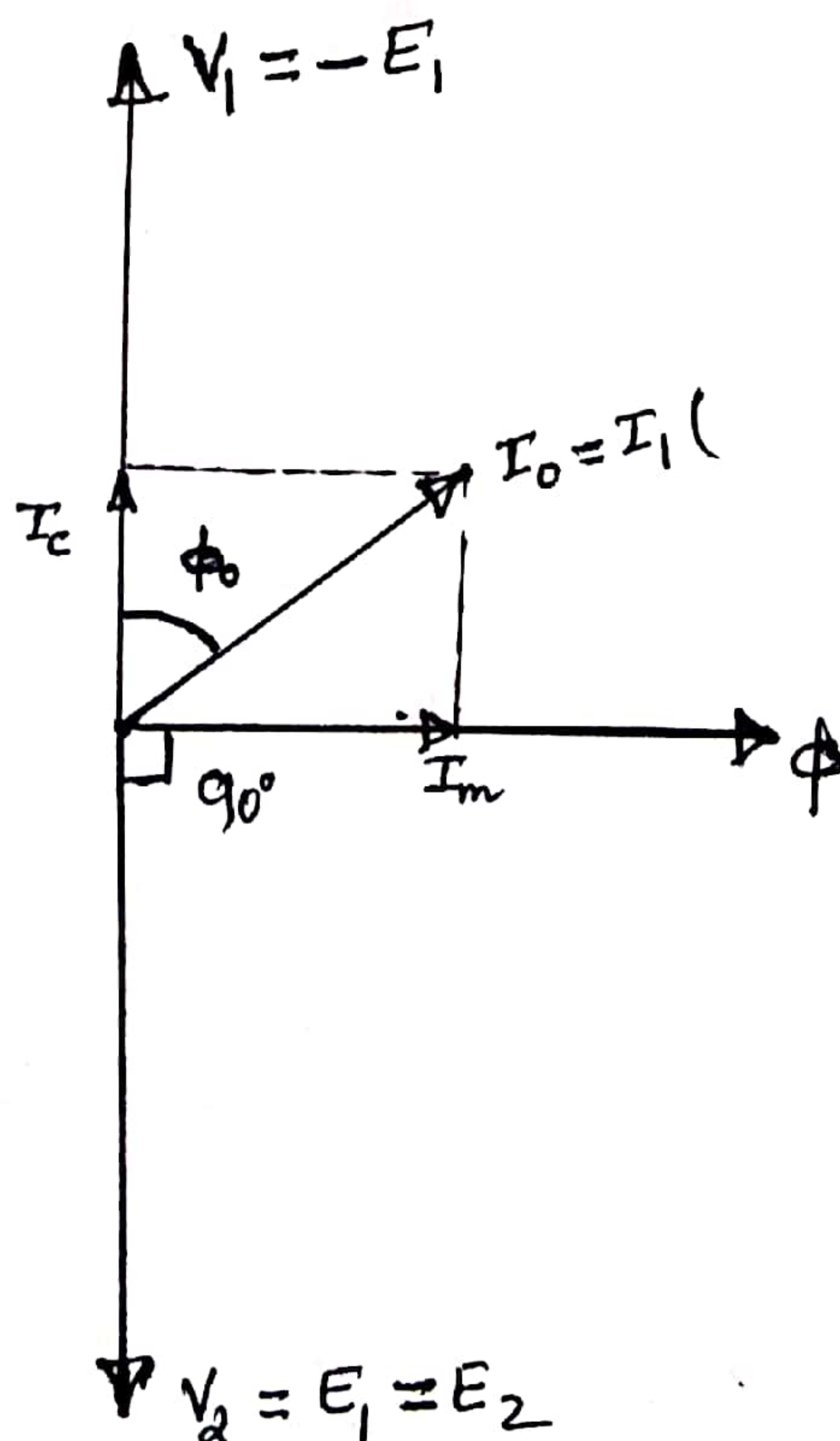$I_c \rightarrow$ core loss current component -



ϕ_0 = No load phase angle

$$I_c = I_0 \cos \phi_0$$

$$I_m = I_0 \sin \phi_0$$

$$I_0 = \sqrt{I_c^2 + I_m^2}$$

for ideal transformer

$$r_1 = 0$$

$$r_2 = 0$$

$$\left. \begin{array}{l} I_1 r_1 = 0 \\ I_2 r_2 = 0 \end{array} \right\} \begin{array}{l} \text{drop} \\ \text{zero} \end{array}$$

No load means secondary terminal is open circuited.

4.13 Phasor diagram of an ideal transformer at load condition

$$\phi = \phi_m \sin \omega t \quad \text{--- (I)}$$

$$E_1 = E_{\max} \sin(\omega t - \frac{\pi}{2}) \quad \text{--- (II)}$$

$$E_2 = E_{\max} \sin(\omega t - \frac{\pi}{2}) \quad \text{--- (III)}$$

$$V_1 = -E_1 \quad \text{--- (IV)}$$

$$\boxed{\begin{aligned} I_1' N_1 &= I_2 N_2 \\ F_1 &= F_2 \end{aligned}}$$

$$\text{Total Primary Current } I_1 = I_1' + I_e \quad \text{--- (V)}$$

I_1' = compensating current- required for maintaining the flux ϕ constant

→ When a load connected across the secondary terminals then according to Lenz's law, the direction of secondary current I_2 should be

such that the secondary mmf $F_2 = N_2 I_2$ is opposite to mutual flux ϕ . This will result reduction in flux ϕ .

To neutralize the demagnetizing effect of secondary mmf, the primary current (I_1) draws ^{extra} current I_1' from the supply and make the mutual flux constant.

Constant flux is necessary for maintaining the value of E_1 & E_2

